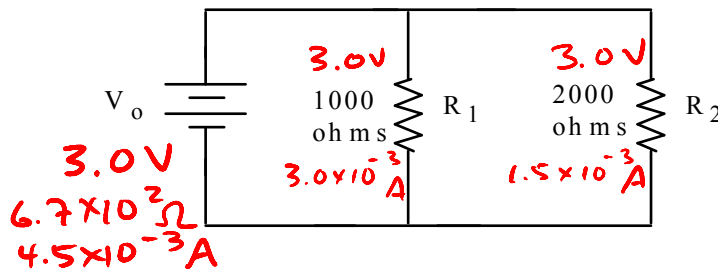


**Example #9:** Consider the following circuit diagram showing two resistors attached in parallel to a battery of two 1.5 V cells. Determine all unknown currents, voltages and resistances.



$$\rightarrow R_o = \left[ \frac{1}{1000} + \frac{1}{2000} \right]^{-1} = 6.7 \times 10^2 \Omega \quad (667)$$

$$\rightarrow I_o = \frac{V_o}{R_o} = \frac{3.0}{667} = 4.5 \times 10^{-3} A$$

$\rightarrow$  voltage drop across each resistor equals voltage gain by battery, so  
 $V_1 = V_2 = 3.0V$

$\rightarrow$  Finally,

$$I_1 = \frac{V_1}{R_1} = \frac{3.0}{1000} = 3.0 \times 10^{-3} A$$

$$I_2 = \frac{V_2}{R_2} = \frac{3.0}{2000} = 1.5 \times 10^{-3} A$$